



Principles of Computer Science I

Prof. Nadeem Abdul Hamid
CSC 120A - Fall 2004
Lecture Unit 6



Computers and Electricity

- Computers represent data using voltage levels along wires
- Signal of 0 to 2 volts is considered "low" and interpreted as binary "0"
- Signal of 2 to 5 volts is "high" and interpreted as binary "1"
- Gate: device that performs a basic operation on electrical signals
 - One or more inputs
 - Single output
- Circuit: combination of gates that perform more complicated task
 - Arithmetic operations
 - Storing values

Describing Gates and Circuits

- Three notations, different but equally expressive
- Boolean expressions
 - Form of algebra invented by George Boole (English mathematician, b. 1815)
 - Mathematical notation for expressing logical functions
- Logic diagrams
 - Graphical representation of circuit
 - Each gate has a specific graphical symbol
 - Gates connected by wires to visually represent logic of entire circuit
- Truth tables
 - List of all possible input combinations for gate/circuit along with corresponding output

Basic Gates

- NOT**
(inverter)

Boolean Expression	Logic Diagram Symbol	Truth Table						
$X = A'$		<table border="1"> <thead> <tr><th>A</th><th>X</th></tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	X	0	1	1	0
A	X							
0	1							
1	0							

- AND**

Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \cdot B$		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X															
0	0	0															
0	1	0															
1	0	0															
1	1	1															

- OR**

Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A + B$		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	1															

Other Basic Gates

- XOR**

Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \oplus B$		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	0															

- NAND**

Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A \cdot B)'$		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

- NOR**

Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A + B)'$		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X															
0	0	1															
0	1	0															
1	0	0															
1	1	0															


Constructing Gates

- Gates can be designed to have three or more inputs
- Gates use one or more transistors to map input to output
- A transistor is a device that acts, depending on the voltage level of an input signal, either as a wire that conducts electricity or as a resistor that blocks the flow of electricity
 - Invented 1947, Bell Labs; revolutionized technology
 - Made of semiconductor material—neither particularly good conductor of electricity, such as copper, nor particularly good insulator, such as rubber
 - Replaced vacuum tubes, which gave off great deal of heat and often failed, requiring replacement

Circuits


- Two general categories
 - In a combinational circuit, the input values explicitly determine the output
 - In a sequential circuit, the output is a function of the input values as well as the existing state of the circuit
- As with gates, we can describe the operations of circuits using three notations
 - Boolean expressions
 - Logic diagrams
 - Truth tables

A Combinational Circuit

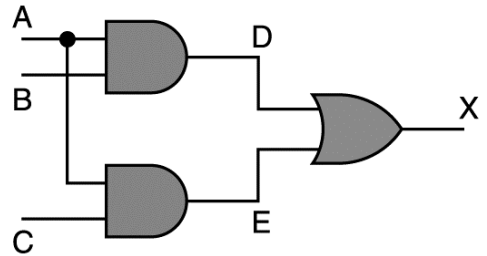

- Boolean expression...
- Truth table...

Another Combinational Circuit

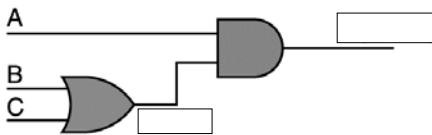

- Boolean expression...
- Truth table...
- Compare the two circuits, Boolean expressions

Boolean Algebra

- Allows us to apply provable mathematical principles to help us design logical circuits
- Properties:


Property	AND	OR
Commutative	$AB = BA$	$A + B = B + A$
Associative	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive	$A(B + C) = (AB) + (AC)$	$A + (BC) = (A + B)(A + C)$
Identity	$A1 = A$	$A + 0 = A$
Complement	$A(A') = 0$	$A + (A') = 1$
DeMorgan's law	$(AB)' = A' \text{ OR } B'$	$(A + B)' = A'B'$

Adders

- At the digital logic level, addition is performed in binary
- Addition operations are carried out by special circuits called, appropriately, adders
- The result of adding two binary digits could produce a *carry value*
- Recall that $1 + 1 = 10$ in base two
- A circuit that computes the sum of two bits and produces the correct carry bit is called a *half adder*

Half Adder

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

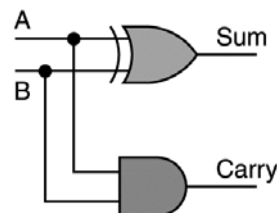

$$\text{sum} = A \oplus B$$


$$\text{carry} = AB$$

Full Adder

- A circuit called a full adder takes the carry-in value into account

Circuits as Memory

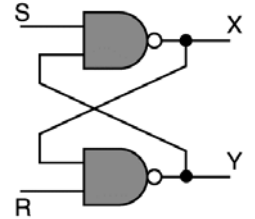- Digital circuits can be used to store information
- These circuits form a sequential circuit, because the output of the circuit is also used as input to the circuit
- Example: The value of X at any point in time is considered to be the current state of the circuit




Integrated Circuits (Chips)

- Piece of silicon on which multiple gates have been embedded
- Silicon pieces are mounted on a plastic or ceramic package with pins along the edges
 - Can be soldered onto circuit boards or inserted into appropriate sockets
- Classified by number of gates:

Abbreviation	Name	Number of Gates
SSI	Small-Scale Integration	1 to 10
MSI	Medium-Scale Integration	10 to 100
LSI	Large-Scale Integration	100 to 100,000
VLSI	Very-Large-Scale Integration	more than 100,000

An SSI Chip

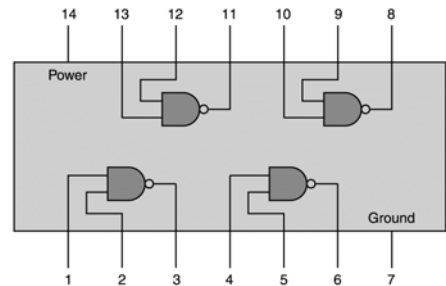

CPU Chips

- The most important integrated circuit in any computer is the Central Processing Unit, or CPU
- Each CPU chip has a large number of pins through which essentially all communication in a computer system occurs

Computer Components

- Consider the following ad

Dell™ Dimension 8100™ Series
The Advanced Performance, Smart Value Desktop

- Intel® Pentium® IV Processor at 866 MHz
- 128MB SDRAM at 1.4 GHz
- 40GB Ultra ATA-100 Hard Drive (7200 RPM)
- 17" (16.0" vis., 28dpi) E770 Monitor
- 16MB ATI Range™ 128 Pro Graphics
- 48X Max CD-ROM Drive
- FREE 8X/4X/24X CD-RW Drive
- SB Live! Value Digital
- FREE 8X/4X/32X CD-RW Drive
- SB Live! Value Digital
- FREE 8X/4X/32X CD-RW Drive
- SB Live! Value Digital

- What does it all mean?

Sizes in Perspective

Power of 10	Power of 2	Value of Power of 2	Prefix	Abbreviation	Derivation
10^{-12}			pico	p	Spanish for little
10^{-9}			nano	n	Greek for dwarf
10^{-6}			micro	μ	Greek for small
10^{-3}			milli	m	Latin for thousandth
10^3	2^{10}	1024	kilo	K	Greek for thousandth
10^6	2^{20}	1,048,576	mega	M	Greek for large
10^9	2^{30}	1,073,741,824	giga	G	Greek for giant
10^{12}	2^{40}	not enough room	tera	T	Greek for monster
10^{15}	2^{50}	not enough room	peta	P	Greek prefix for five

Jargon

- MHz - megahertz / GHz - gigahertz
 - Hertz = cycles per second
- SDRAM - static dynamic random access memory (main memory): 128×2^{20} bytes
 - Can be accessed at 1.4GHz (cycles per second)
- Disk drive:
 - Ultra ATA-100 - type of interface/transfers data at 100MB/second
 - Spins at 7200 revolutions per minute
- Monitor
 - 15" visible 28 dot pitch
- CDROM, CD-RW
 - ROM - read-only-memory
 - DVD: digital versatile disk
- Sound card, speakers
- Modem
 - 56K: 56,000 bytes per second
- Software, services...

Dell™ Dimension 8100™ Series
The Advanced Performance, Smart Value Desktop

- Intel® Pentium® IV Processor at 800 MHz
- 20GB 5400RPM 8.0 Drive
- 40GB Ultra ATA-100 Hard Drive (7200 RPM)
- 17" (16.0" vis, 28dot) CRT Monitor
- 10000 BT Ethernet™ 10/100mbps
- 4X Max CD-ROM Drive
- FREE DVD/CDRW CD-RW Drive
- 28 LPM Video Digital
- Audio: LiveRange™ ACS-342™
- Speakers with Subwoofer
- V.90 56K Creative® PCI Telephony
- Modem for Windows®
- 4GB Memory (8GB 3001)
- MSN Windows® Me
- 3-Yr Limited Warranty
- 1-Yr Next Business Day Service
- 1 Year of Dell™ Support by MSN®
- Internet Access Included